

Probability Hardware Assignment

Name -: Kunchala Karthik
Roll no -: CS22BTECH11034

Abstract—In this assignment we have made a Random number generator using shift registers

COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K Ω	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

TABLE 0
COMPONENTS USED

PROCEDURE

- 1) We connected the 555 timer circuit according to the figure ??

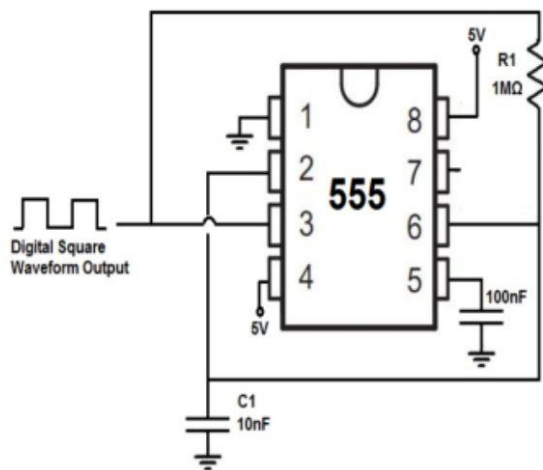


Fig. 1. Connection in 555 timer circuit

- 2) Then we connected Clock output of 555 timer circuit to the clock signal of D-Flip flops

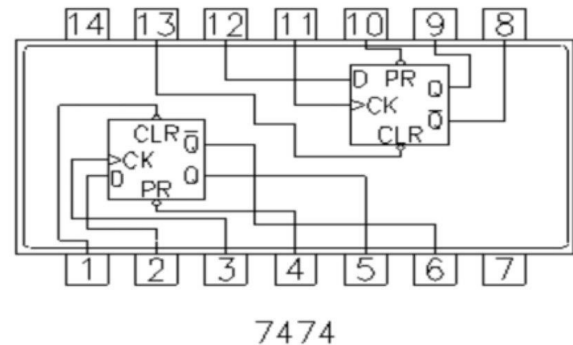


Fig. 3. Connection in 7474 IC

- 3) Now we make the circuit for shift registers using a 4 D-Flip flops (using two 7474 IC's)
- 4) Then we connected XOR gate (7486 IC) according to the figure ??

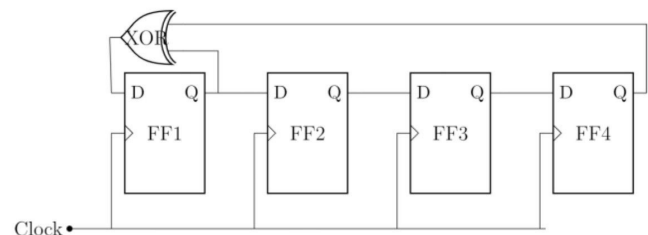


Fig. 4. Connection in XOR gate

- 5) then we connected the decoder (7447 IC) and connected its A,B,C,D with Q_0, Q_1, Q_2, Q_3 respectively as per the figure ??
- 6) Then we connected The seven segmented display and then connected it with the dceoder (7447 IC) according to the table ?? and the figure ??
- 7) We connected all the independent parts with each other and then connected the power source

OUTPUT

Output was changing digits on the seven segment display the output is shown in figure ??



Fig. 5. Connection in Decoder gate

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 6. Connection of seven segmented display with decoder

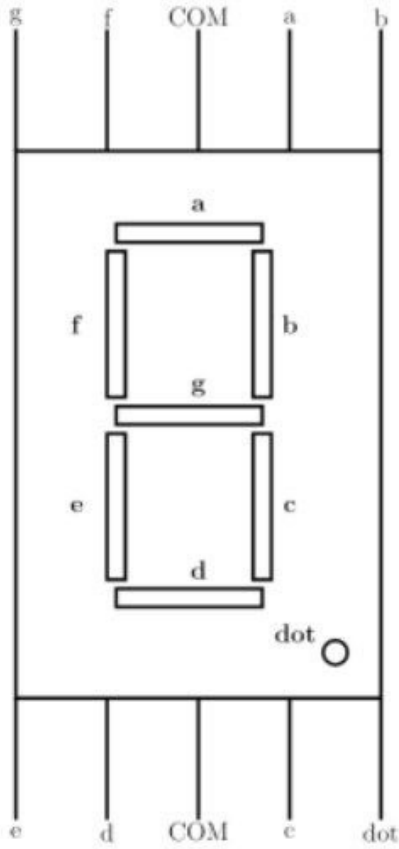


Fig. 6. Seven segmented display

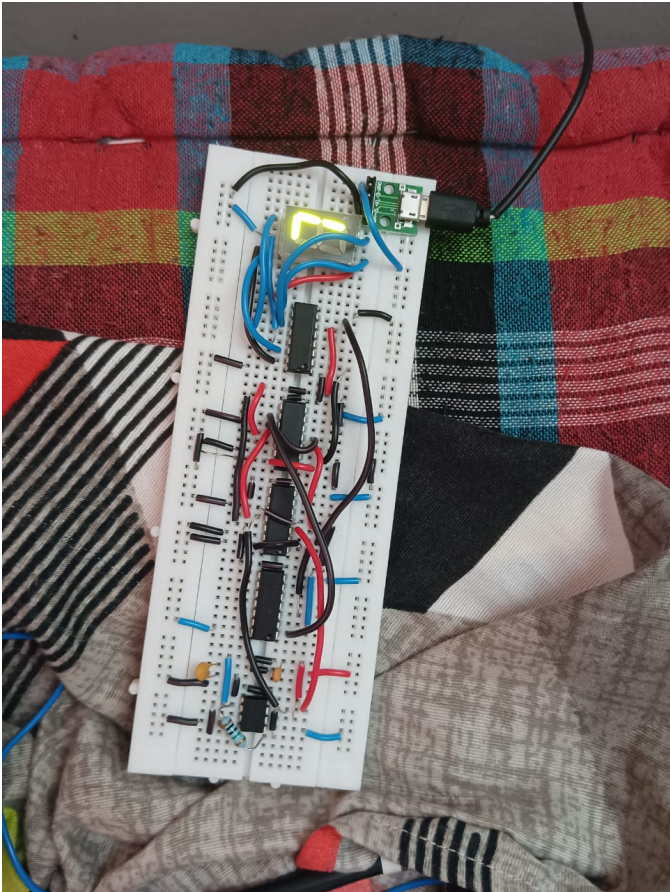


Fig. 7. output